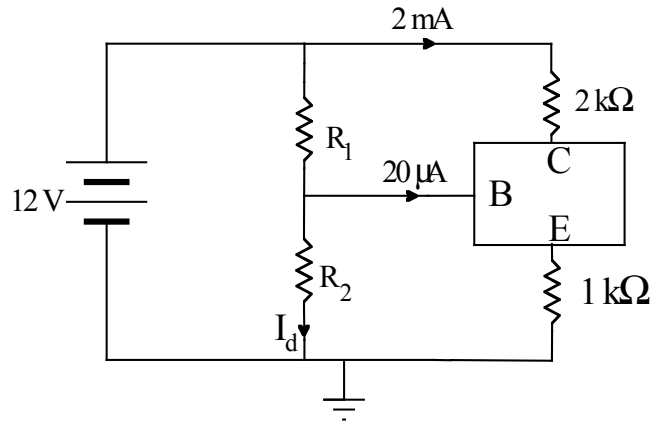


### Physics 517/617 Homework 3 (Due July 26<sup>th</sup>)

1) A “black box” with three terminals labeled E, B, and C is connected in the circuit shown at the right. (a) Calculate  $V_C$  and  $V_E$ . (b) If terminal “B” is 0.6 V higher in voltage than terminal E, calculate  $R_1$  and  $R_2$  (in terms of  $I_d$ ), assuming that  $I_d$  is very large compared to the  $20 \mu A$  flowing into the B terminal and can be neglected in setting up a voltage divider. (This “black box” is a silicon NPN transistor and C, B, and E will refer to the collector, base and emitter terminals when we study those devices).



2) Use the diode equation,  $I_D = I_0 \left( e^{\frac{qV_D}{kT}} - 1 \right)$ , for what follows. Consider a diode with a “bias”

current and voltage,  $I_{bias}$  and  $V_{bias}$ . (these are related by the diode equation). Consider now adding a small *additional* “signal” voltage,  $\delta v$ , across the diode which will in turn drive a small additional current  $\delta i$ . Show (use differential calculus) that the “differential resistance” relating these,

i.e.  $r \equiv \frac{\delta v}{\delta i}$  is given by:  $r = \frac{1}{38.9 \cdot I_{bias} (A)}$  --- or --- if the bias current is measured in mA  $r = \frac{25.7}{I_{bias} (mA)}$ .

3) Using one or more op-amps, design a summing amplifier that given inputs  $v_a$ ,  $v_b$ ,  $v_c$ , and  $v_d$  produces the sum:  $v_{out} = 8v_a + 4v_b + 2v_c + v_d$ .